

interferences.
 Process of using reactive elements to diminish the distortion caused by ...

18/01/2022

Return to text
 Question

1) Design Assumption

↓
 Design Equations

↓
 Design Calculations

↓
 Prototype

(c) → The presence of design specifications imply the presence of design assumptions.

Assumption 1
 (1) $V_{CE} \approx \frac{50}{100} V_{CC}$

(a) $V_{CE} = 50\% \text{ of } V_{CC}$

* V_{CC} is the rail voltage.

Assumption 2:
 Voltage across the emitter

$$V_E = \frac{I_E}{I_{E0}} \times V_{CC}$$

To obtain amplification,

$$V_{CE} = \frac{40}{100} \times V_{CC}$$

(c) The design equation will stem directly from the design assumptions:

(1) $V_{CE} = 0.5 V_{CC}$

(2) $V_{PC} = 0.4 V_{CC}$

(3) $V_E = 0.1 V_{CC}$

(4) $\beta = h_{FE} = \frac{I_E}{I_B}$
 (Current gain)

the Design equation


* Two kinds of analysis performed:

(1) D.C & A.C analysis

* To perform DC analysis we have to first draw the DC equivalent circuit.

→ capacitors must be open circuited and all inductors must be shorted.

(iii) DC Equivalent Circuit:

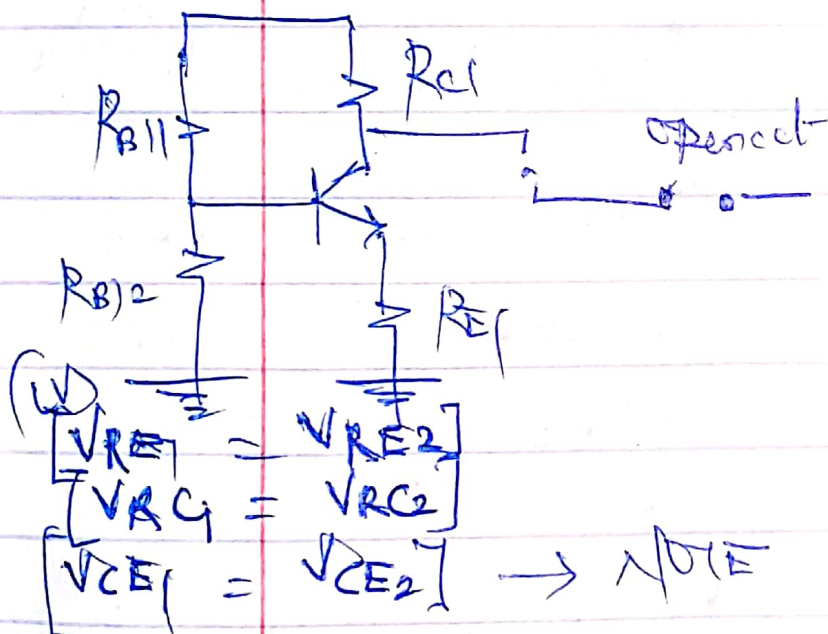

From the given questions

$$V_{CC} = 12V$$

$$V_{CE} = \frac{50}{100} (12V) = 6V$$

→ Design Calculations

$$\therefore V_{CE1} = V_{CE2} = 6V$$

$$V_{RC} = \frac{40}{100} (12) = 4.8V$$

$$\therefore V_{RC1} = V_{RC2} = 4.8V$$

$$V_{RE} = \frac{10}{100} (12) = 1.2V$$

$$\therefore V_{RE1} = V_{RE2} = 1.2V$$

$$(v) \frac{12 - 4.8}{10mA} = R_{C1}$$

$$\rightarrow R_{C1} = \left(\frac{V_C}{I_C} \right) = 720\Omega$$

NOTE: Do not assume that $I_C \approx I_E$.

$$R_E = \frac{V_E}{I_E} = \frac{V_E}{I_B + I_C}$$

$$\beta = \frac{I_C}{I_B}$$

$$\rightarrow I_B = I_C / \beta$$

Given current gain (β) = 100

$$I_B = \frac{10mA}{100} = 0.1mA$$

$$I_B + I_C = 10 + 0.1 = 10.1mA$$

$$\rightarrow R_E = \frac{V_E}{10.1mA} = \frac{1.2V}{10.1mA}$$

$$R_E = 0.118K\Omega$$

Note: $\begin{cases} R_{C1} = R_{C2} \\ R_{E1} = R_{E2} \end{cases}$

(vi) $I_{B1} = \frac{V_{E1}}{R_{E1}} = I_{B2} = \frac{V_{E2}}{R_{E2}}$

$I_B = I_E / \beta = I_{B1} = I_{B2}$

$= 0.1 \text{ mA}$

(vii) for silicon transistors, $V_{BE} = 0.7 \text{ V}$

$V_{RB12} = V_{BE} + V_{RE1}$

$= 0.7 + 1.2$

$V_{RB12} = 1.9 \text{ V}$

$\underline{V_{RB12} = V_{RB22} = 1.9 \text{ V}}$

(viii) I_{RB12} is usually 10 times the base current

$(I_B) \rightarrow I_{RB12} = 10 I_B$

$\rightarrow I_{RB12} = I_{RB22} = 10 I_B$

$= 10 (0.1 \text{ mA})$

$= \underline{1 \text{ mA}}$

(ix) $R_{B12} = \frac{V_{RB12}}{I_{RB12}}$

$R_{B22} = \frac{V_{RB22}}{I_{RB22}}$

And $R_{B12} = R_{B22}$

$\rightarrow R_{B12} = R_{B22} = \frac{1.9 \text{ V}}{1 \text{ mA}}$

$R_{B12} = R_{B22} = \underline{1.9 \text{ k}\Omega}$

(x) $V_{CC} = V_{RB11} + V_{RB12}$

$\therefore V_{RB11} = V_{CC} - V_{RB12}$

$\therefore V_{RB11} = 12 - 1.9$

$V_{RB11} = \underline{10.1 \text{ V}}$

And $\underline{V_{RB11} = V_{RB21} = 10.1 \text{ V}}$

(xi) $I_{RB11} = I_B + I_{RB12}$

$= 0.1 + 1$

$\underline{I_{RB11} = 1.1 \text{ mA} = I_{RB21}}$

(xii) $R_{B11} = \frac{V_{RB11}}{I_{RB11}} = R_{B21}$

$$R_{B1} = R_{B2} = \frac{10.1V}{1mA} = 9.18k\Omega$$

→ Marks the end of the DC Analysis.

Onto the AC Analysis 2

(Xiii) To draw the AC equivalent circuit:

→ For AC equivalent circuit,

Capacitors → short circuit

Inductors → open circuit

→ The AC equivalent circuit will help to calculate the value of the capacitor.

C_{IN1} → i/p coupling capacitor for 1st stage


C_{IN2} → i/p coupling capacitor for 2nd stage

C_{E1} } Bypass capacitors
 C_{E2} }

C_{OUT} → o/p coupling capacitor

$$[C_{IN1} \approx C_{IN2}]$$

Draw AC equivalent circuit:

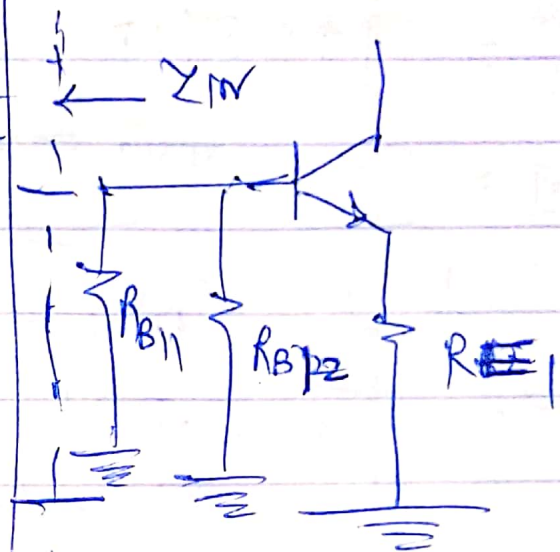

$$Z_{IN} = (R_{B1} \parallel R_{B2} \parallel \beta r_e)$$

(Xiv) $C_{IN1} = \frac{1}{2\pi f_{3dB} X_C}$
→ X_C is usually not given; so, assumption works:

$$[X_C \approx \frac{1}{10} R_E]$$

from recall $R_E = 0.118k\Omega$

$$X_C \approx \frac{1}{10} (0.118k\Omega)$$

$$X_C = 11.8\Omega$$

→ f used is frequency at 3dB = 30MHz

$$C_M = \frac{1}{2\pi(30\text{MHz})(11.8)}$$

$$C_M = 449.59 \text{ pF}$$

$$C_M = C_{E2} = 449.59 \text{ pF}$$

To calculate C_{IN} , we obtain the input impedance of the ckt:

$$C_{IN} = \frac{1}{2\pi f_{3dB} Z_{IN}}$$

Z_{IN} : input impedance as seen by the source (which is the signal generator).

$$Z_{IN} = (R_{B1} \parallel R_{B2} \parallel R_{EE}) \times \beta r_e$$

βr_e :

r_e - base-emitter internal resistance

$$[r_e = 25\text{mV} / I_E] \text{ or } [26\text{mV} / I_E]$$

$$\rightarrow r_e = \frac{25\text{mV}}{10\text{mA}}$$

$$r_e = 2.5 \text{ m}\Omega$$

$$Z_{IN} = 247.5 \Omega$$

$$\times (R_{B1} \parallel R_{B2} \parallel R_{EE})$$

$$\rightarrow Z_{IN} = 27.17 \text{ k}\Omega$$

$$C_{IN} = \frac{1}{2\pi(30\text{MHz})(27.17\text{k}\Omega)}$$

$$= 0.1953 \text{ nF} = C_{IN2}$$

$$C_{OUT} = \frac{1}{2\pi f_{3dB} Z_{OUT}}$$

$$\text{And } Z_{OUT} = R_C = 720 \Omega$$

$$C_{OUT} = \frac{1}{2\pi f_{3dB} R_C}$$

$$C_{OUT} = 7.37 \text{ pF}$$

These values can then be taken to find f_{L1} and f_{L2} and then

Further built on a
breakpoints — and then on
a PCB.


(XIV) The estimated frequency
response is simply the
amplifier frequency response
(or Bode plot)
diagram.

(XV) Simply comment on the
efficiency of the class
A amplifier (eff = 50%)

(XVI) An oscillator is an
amplifier with a feedback
loop.

→ Take the Colpitts oscillator
feedback path
and connect it to the
input of the 2nd stage.

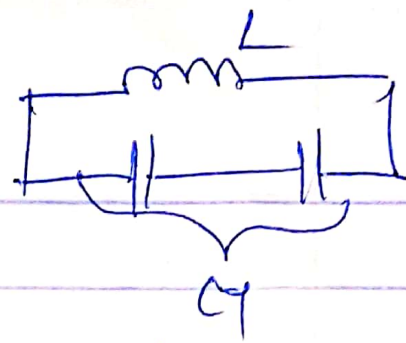(XVII) $\tau = 1/2\pi f$
 $f = 90 \text{ MHz}$ • (Calc. L.)



Colpitts
LC
tank

$$f = \frac{1}{2\pi\sqrt{LC}}$$

$$\rightarrow 2\pi f = \frac{1}{\sqrt{LC}}$$

$$\left(\frac{1}{2\pi f}\right)^2 = LC$$

$$\text{or } L = \frac{1}{C} \left(\frac{1}{2\pi f}\right)^2$$

$$L = 0.2606 \mu\text{H}$$

(XIX) A response having
an exponential growth
upwards and downwards.

(XX) The frequency will
fit very perfectly.
b/c ...?

Next Class: The
remaining questions will
be treated