

Course : CPB 435 - Prototyping Techniques

Group No: 5

Group Specification : 7VDC

Group Members

1	Adebiyi Seminire Deborah	170408031
2	Oloton Joshua Osayanede	170408033
3	Abah Success Monday	170408034
4	Ben-Njoku Chioma James	160408042
5	Awoyemi Abiola	170408037

DESIGN OF A TWO-STAGE CLASS A - CAPACITOR COUPLED RADIO FREQUENCY AMPLIFIER

① Design Assumptions

- Voltage Across terminal collector V_{CE} must be half of the rail Voltage V_{CC}
- Voltage Across emitter V_E must be 10% of rail Voltage
 $V_E = 10\% \text{ of } V_{CC}$
- Voltage across the collector resistor V_{RC} is 40% of rail Voltage
 $V_{RC} = 40\% \text{ of } V_{CC}$
- The Transistor is Biased in a linear region

② Component Calculations

- (i) $V_{CC} = 7V$
- (ii) $V_{CE} = 0.5 V_{CC} = 3.5V$
 $V_{CE1} = V_{CE2} = 3.5V$
- (iii) $V_{RC} = 0.4 V_{CC} = 0.4 \times 7 = \cancel{0.7V} 2.8V$
- (iv) $V_{RE1} = V_{RE2} = 0.1 V_{CC} = 0.7V$
- (v) $R_C = \frac{7 - 2.8}{10mA} = 0.42K\Omega = \frac{V_{CC} - V_{RC}}{I_C}$
 $I_C = 10mA \quad R_C = 0.42K\Omega$
- (vi) $R_E = \frac{V_E}{I_E} = \frac{V_E}{I_C + I_B} = ?$

$$H_{FE} = 100$$

$$I_C = H_{FE} \times I_B$$

$$I_B = \frac{10 \times 10^{-3}}{100} = 0.1 \text{ mA}$$

$$I_B = 0.1$$

$$\therefore R_E = \frac{0.7}{(10 + 0.1) \times 10^{-3}} = 69.30 \Omega$$

$$(vii) \quad R_C: V_{RB12} = V_{BE} + V_{RE1}$$

$$V_{BE} (\text{Silicon}) = 0.7 \text{ V}$$

$$V_{RB12} = 0.7 + 0.7 = 1.4 \text{ V} = V_{RB22}$$

$$(viii) \quad I_{RB12} = I_{RB22} = 10 I_B = 10 \times 0.1 = 1 \text{ mA}$$

$$(ix) \quad R_{B12} = \frac{V_{RB12}}{I_{RB12}} = 1.4 \text{ k}\Omega$$

$$R_{B22} = 1.4 \text{ k}\Omega$$

$$(x) \quad V_{RB21} = V_{RB11} = 7 - 1.4 = 5.6 \text{ V}$$

$$(xi) \quad I_{RB11} = I_B + I_{RB12} \\ = 0.1 + 1 = 1.1 \text{ mA}$$

$$(xii) \quad R_{B11} = R_{B21} = 5.6 / 1.1 = 5.09 \text{ k}\Omega$$

(2cm) $C_{E1}, C_{E2}, C_{in}, C_{out}$

$$C_{E1} = \frac{1}{2\pi f X_c}$$

$$X_c = \frac{1}{2\pi f c} = \frac{R_E}{10} = \frac{69.30}{10} = 6.930 \Omega$$

$$f = 30 \times 10^6 \text{ Hz}$$

$$C_{E1} = \frac{1}{2\pi \times 30 \times 10^6 \times 6.930} = 0.765 \text{ nF}$$

$$C_{E1} = C_{E2} = 0.765 \text{ nF}$$

$$V_T = 26 \text{ mV}$$

$$r_e = \frac{V_T}{I_c + I_b} = \frac{26 \times 10^{-3}}{10.1 \times 10^{-3}} = 2.574 \Omega$$

$$Z_{in} = (5.09 \times 10^3 // 1.4 \times 10^3 // 69.30) \times 100 \times 2.574$$

$$Z_{in} = 16.77 \times 10^3 \Omega$$

$$C_{in1} = C_{in2} = \frac{1}{2\pi \times 30 \times 10^6 \times 16.77 \times 10^3}$$

$$C_{in1} = C_{in2} = 0.3163 \text{ pF}$$

$$C_{out} = \frac{1}{2\pi \times 30 \times 10^6 \times 0.42 \times 10^3} = 0.01263 \text{ nF}$$



